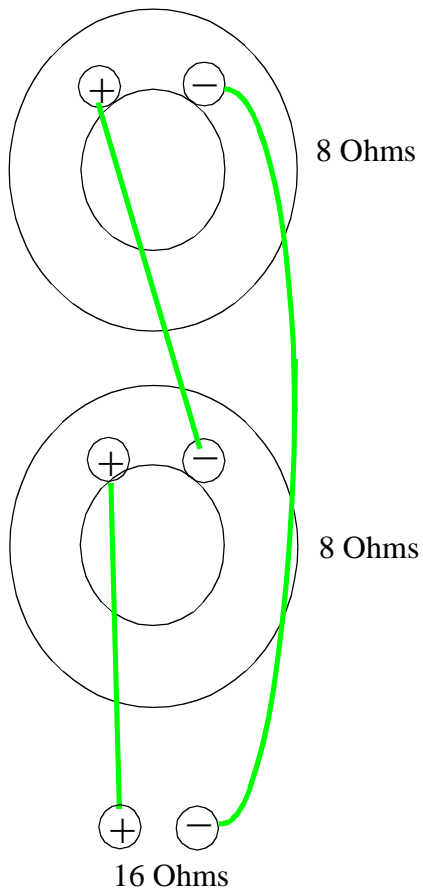


Series Wiring for 2x12 Cab


Series Wiring



Two 8-Ohm speakers
wired in series to yield a
total load of 16 Ohms.

Formulae:
 $2 \times 8 = 16$
 $8 + 8 = 16$

Schematic View*

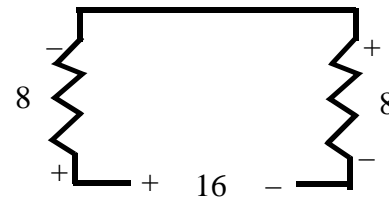

* Polarity is shown *only* to indicate positive
and negative speaker terminals.

